

Lab 7

Andrew Walker


Down Counter 3 to 0

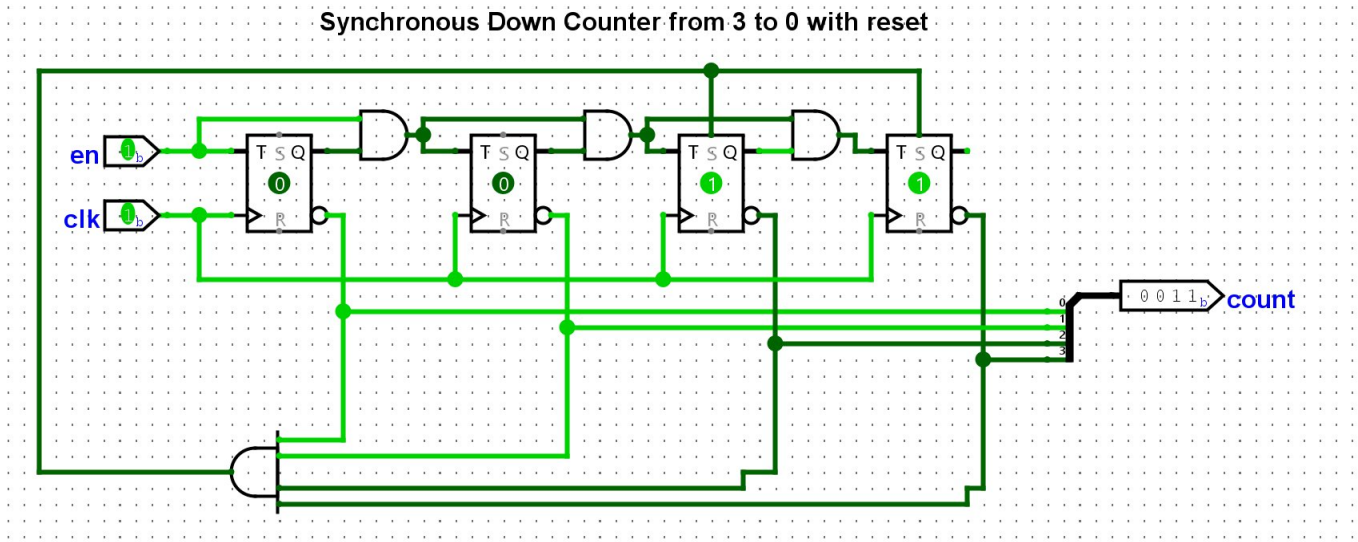


Down Counter 3 to 0 video

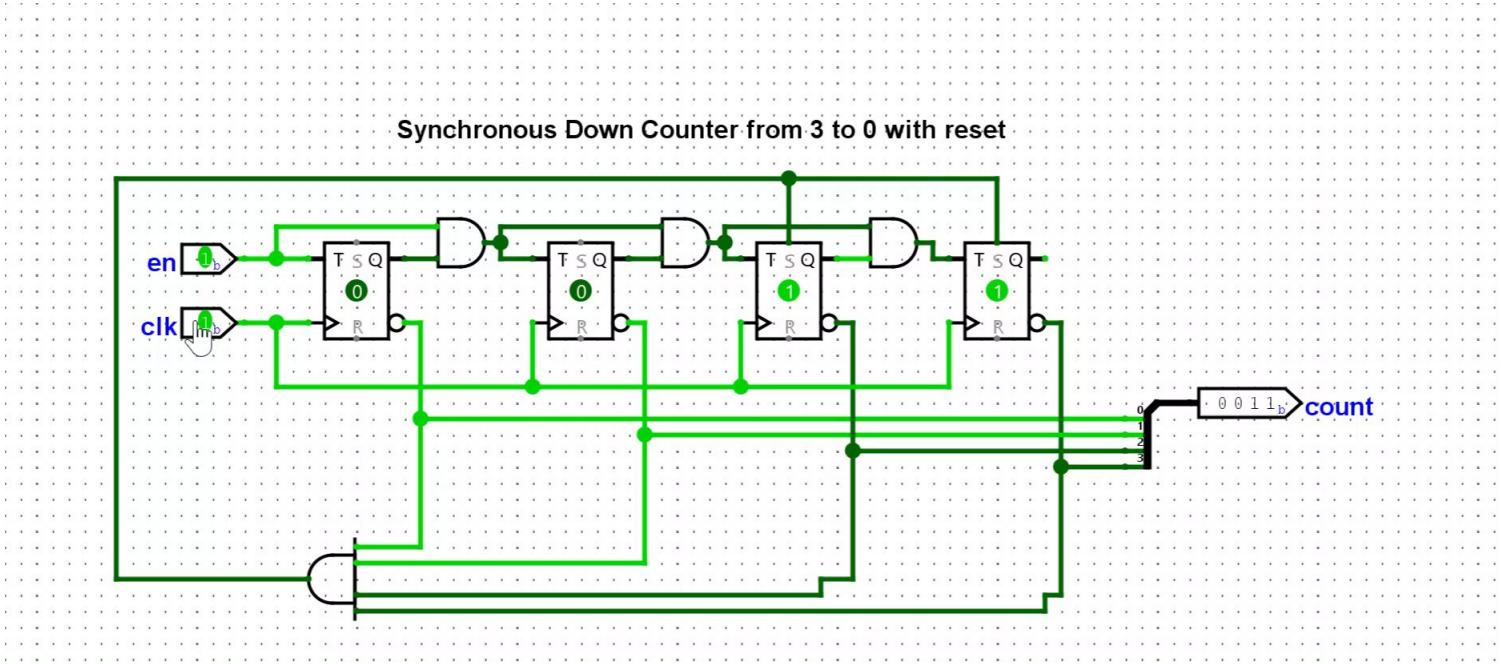


FSM Logic and Tables

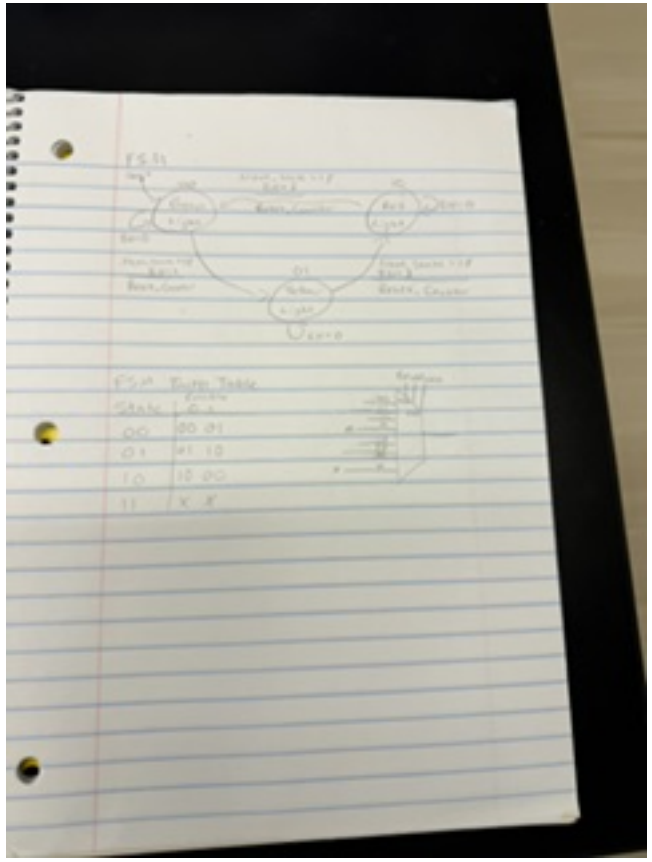


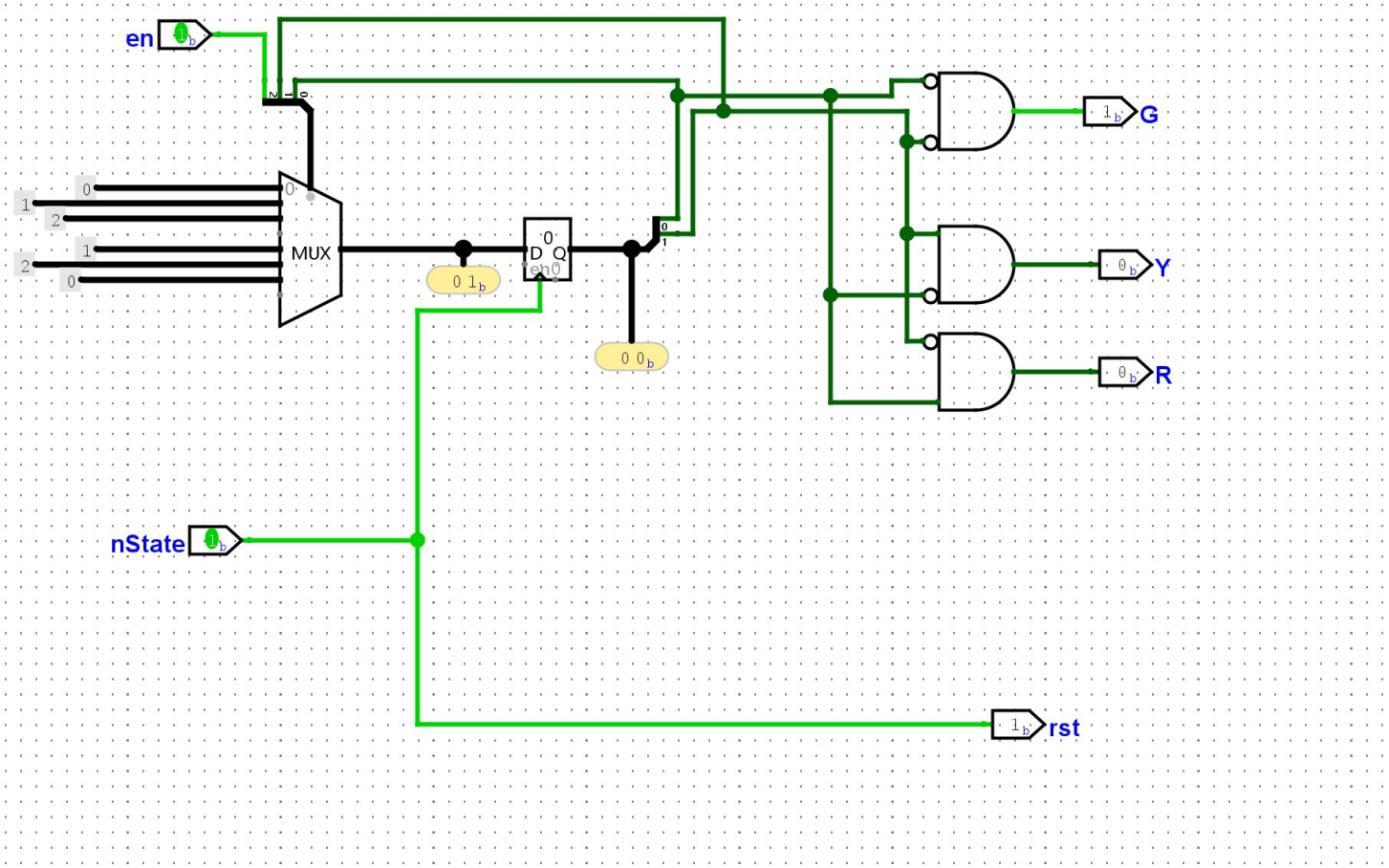

FSM video

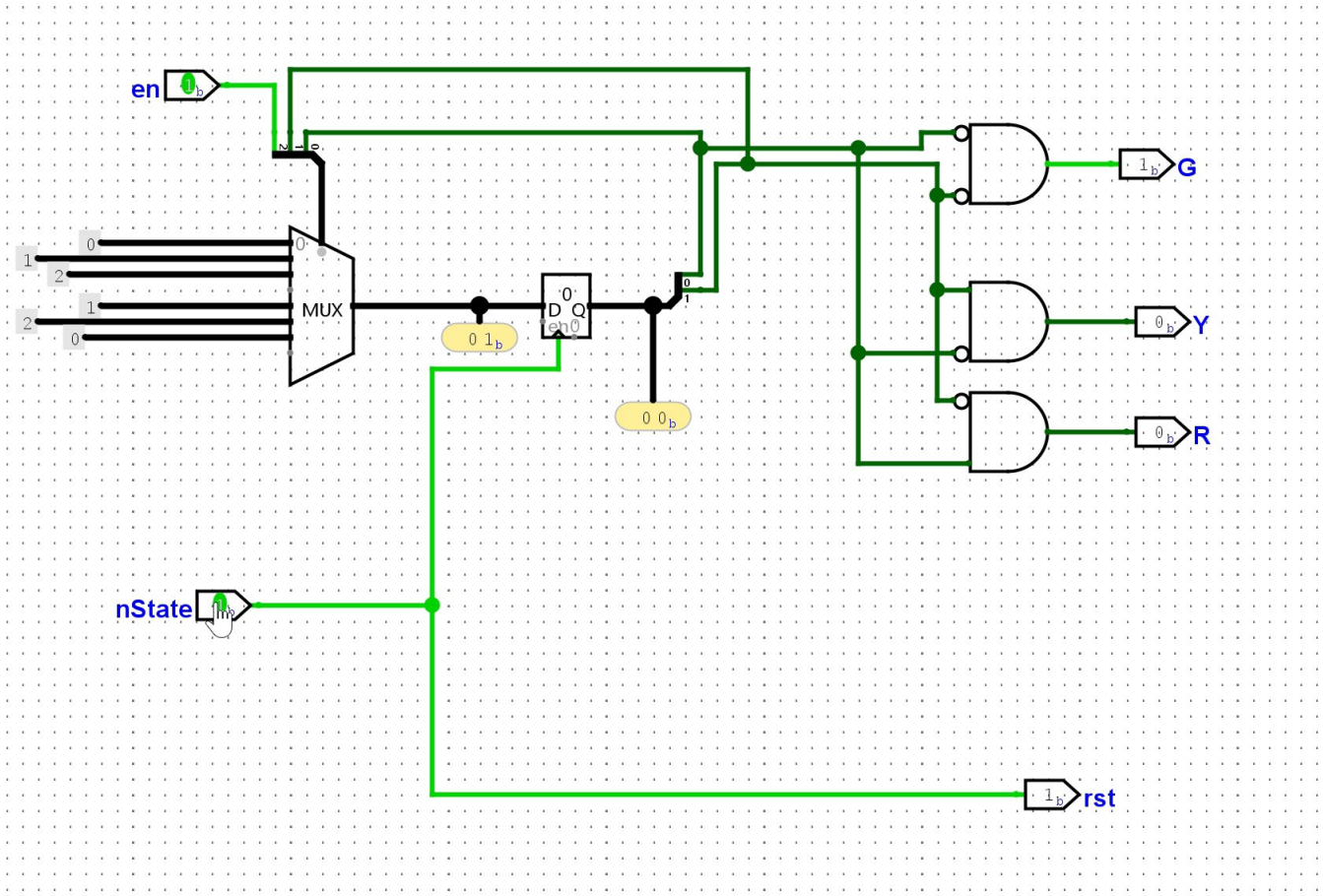

Stop Light

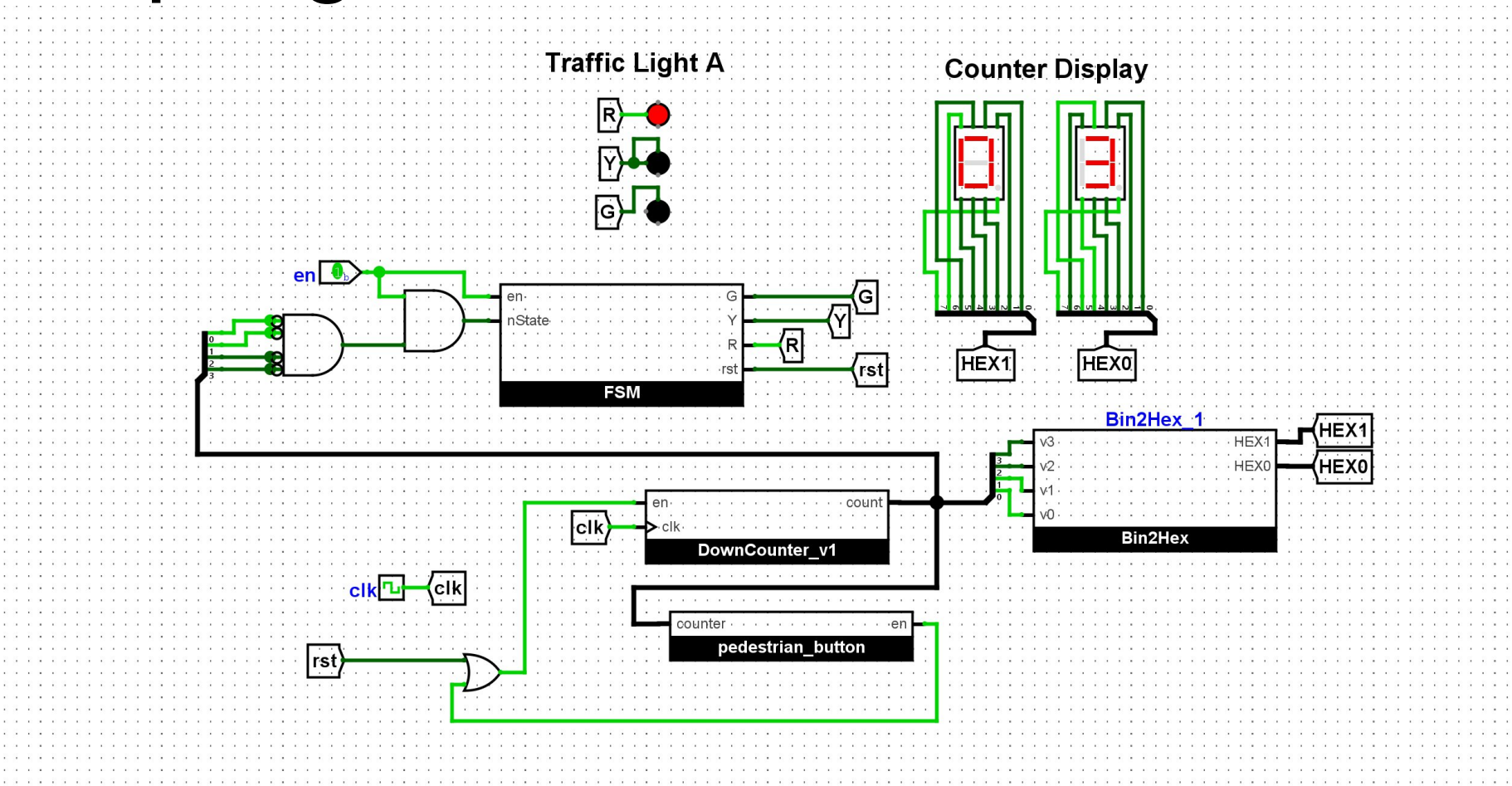
Traffic Light A
Counter Display
R
Y
G
en
nState
FSM
rst
HEX1
HEX0
Bin2Hex_1
v3
v2
v1
v0
Bin2Hex
clk
DownCounter_v1
count
pedestrian_button
counter

Stop Light Video

